

## Introduction & Safety

### TWO FACTORS WHICH DETERMINE IF A SHOCK IS FATAL

The amount of current entering the body.

Amp CAN BE lethal.

\_\_\_\_\_ through the body. A current path through the \_\_\_\_\_ is usually FATAL.

What would you do if you observed someone being electrocuted? \_\_\_\_\_

---

---

## INTRODUCTION TO ELECTRICITY


### LAW of Electrostatic Force:

\_\_\_\_\_ Charges Attract.

\_\_\_\_\_ Charges Repel.


Conductor: A material with (loose or tightly) bound electrons

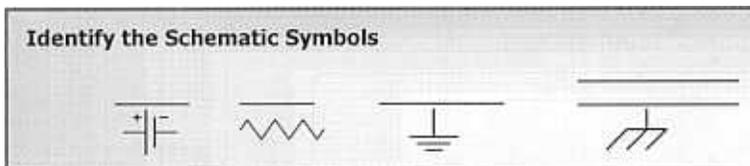Insulator: A material with (loose or tightly) bound electrons


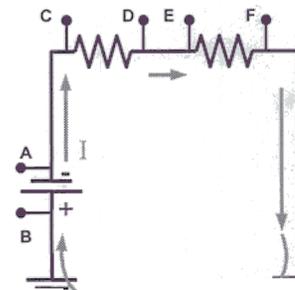
### Solve for the following:

Point c is \_\_\_ with respect to point e  
Point f is \_\_\_ with respect to point c  
Point e is \_\_\_ with respect to point f



## Numerical Notations

Solve the following

$$5^3 =$$

$$3^3 =$$

$$3^5 =$$

### Exponents & The powers of 10


$$100,000 =$$

$$10^4 =$$

$$1,000 =$$

$$10^2 =$$

$$10^0 =$$

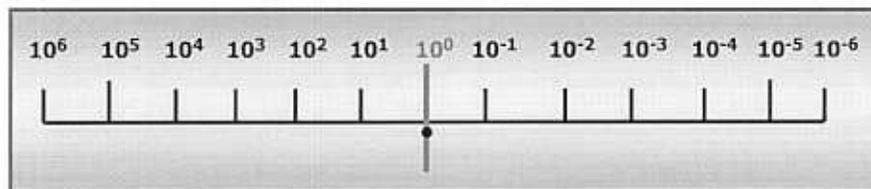

$$234,000 = 234 *$$

$$234,000 = 23.4 *$$

$$234,000 = .234 *$$

$$2 * 10^6$$

$$15 * 10^4 = \underline{\hspace{2cm}}$$

$$10 * 10^6 = \underline{\hspace{2cm}}$$

Converting a Fraction, to a NEGATIVE Pwr of 10, the Decimal is moved            and is indicated in the exponent of the Pwr of 10.

Converting a NEGATIVE Pwr of 10, to a Fraction, the Decimal is moved            as is indicated in the exponent of the Pwr of 10

Indicate the directions of the arrows in relation to the letters given

D R I L

\_\_\_\_\_

When ADDING the Powers of 10 the Exponents must be.

$$26 * 10^3 + 26 * 10^3 =$$

$$5 * 10^2 + 15 * 10^2 =$$

$$6 * 10^3 + 120 * 10^2 =$$

$$65 * 10^4 + 22 * 10^6 =$$

SUBTRACTION; All rules apply as w/ Addition.

$$64 * 10^3 - 26 * 10^3 =$$

$$25 * 10^2 - 15 * 10^2 =$$

$$600 * 10^3 - 120 * 10^2 =$$

$$28 * 10^4 - 22 * 10^6 =$$

Multiplying the powers of 10, the Exponents must be \_\_\_\_\_ in the problem, to get the Exponent in the solution. PROVIDED the Polarities are the same

$$14 * 10^3 * 10 * 10^3 =$$

$$58 * 10^3 * 2 * 10^3 =$$

$$30 * 10^3 * 3 * 10^3 =$$

$$25 * 10^3 * 5 * 10^3 =$$

When the Exponents Polarities are NOT the same, Multiplying the powers of 10, the Exponents must be \_\_\_\_\_ in the problem, to get the Exponent in the solution.

$$14 * 10^{-2} * 10 * 10^3 =$$

$$6 * 10^7 * 2 * 10^{-3} =$$

$$8 * 10^{-4} * 3 * 10^7 =$$

$$25 * 10^3 * 5 * 10^{-3} =$$


**Division: The rule for solving for the exponent is: Cross the line change the ?**

$$\frac{16 * 10^3}{4 * 10^{-4}}$$

$$\frac{24 * 10^3}{6 * 10^{-4}}$$

$$\frac{45 * 10^3}{5 * 10^{-4}}$$

$$\frac{64 * 10^3}{8 * 10^{-4}}$$

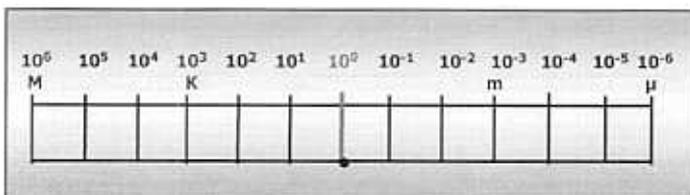

Converted the following to a prefix value.

$14 * 10^3 = \underline{\hspace{2cm}}$

$56 * 10^4 = \underline{\hspace{2cm}}$

$214 * 10^6$

$14 * 10^{-3} = \underline{\hspace{2cm}}$

$14 * 10^{-8} = \underline{\hspace{2cm}}$

$14 * 10^{-6} =$

Solve the following problems, Answer in Prefix Value


$5K + 10K = \underline{\hspace{2cm}}$

$15K + 22K = \underline{\hspace{2cm}}$


$10K + 90K = \underline{\hspace{2cm}}$  or

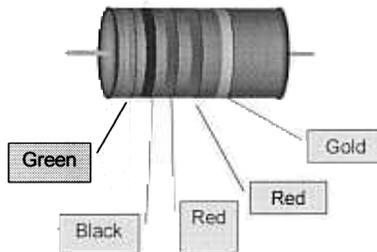**DC: Ohms Law**

**Resistance:**  
**Tolerance:**  
**Amount of tolerance:**  
**Upper limit:**  
**Lower limit:**



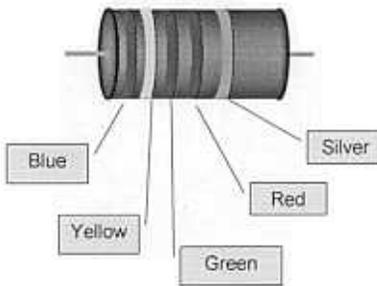**Resistance:**  
**Tolerance:**  
**Amount of tolerance:**  
**Upper limit:**  
**Lower limit:**



**Resistance:**  
**Tolerance:**  
**Amount of tolerance:**  
**Upper limit:**  
**Lower limit:**



**5 Band resistors**  
 The 1<sup>st</sup> color band indicates \_ digit.  
 The 2<sup>nd</sup> color band indicates \_ digit.  
 The 3<sup>rd</sup> color band indicates \_ digit.  
 The 4<sup>th</sup> color band indicates \_\_\_\_\_.  
 The 5<sup>th</sup> color band indicates \_\_\_\_\_.

**DC: Ohms Law**

**Voltage:** Electromotive Force, EMF, Is a Difference in \_\_\_\_\_  
{ or force } between two points + & - That causes electrons to move  
or flow in a conductor

The letter symbol for voltage is:

The unit of measure for voltage is:

**CURRENT** Is the MOVEMENT OF ELECTRONS From the most \_\_\_\_\_, to the  
most \_\_\_\_\_ point in the circuit.

The letter symbol for current is:

Unit of Measure is:

**Resistance:** Is the \_\_\_\_\_ Resistance controls the flow of  
current.

The letter symbol for Resistance is:

Unit of Measure is:

\* = **Voltage Applied**

\* = **Current**

\* = **Resistance**

Fill in the blanks for Ohms Law


$E / R = I$        $R * I = E$        $I * R = E$        $E / R = I$

$E / R = I$        $I / R = E$        $R * I = E$        $E / R = I$

## Finding Voltage Drops

As current flows, it enters a resistor \_\_\_\_\_, and leaves that same resistor \_\_\_\_\_ in respect to the point of entry.

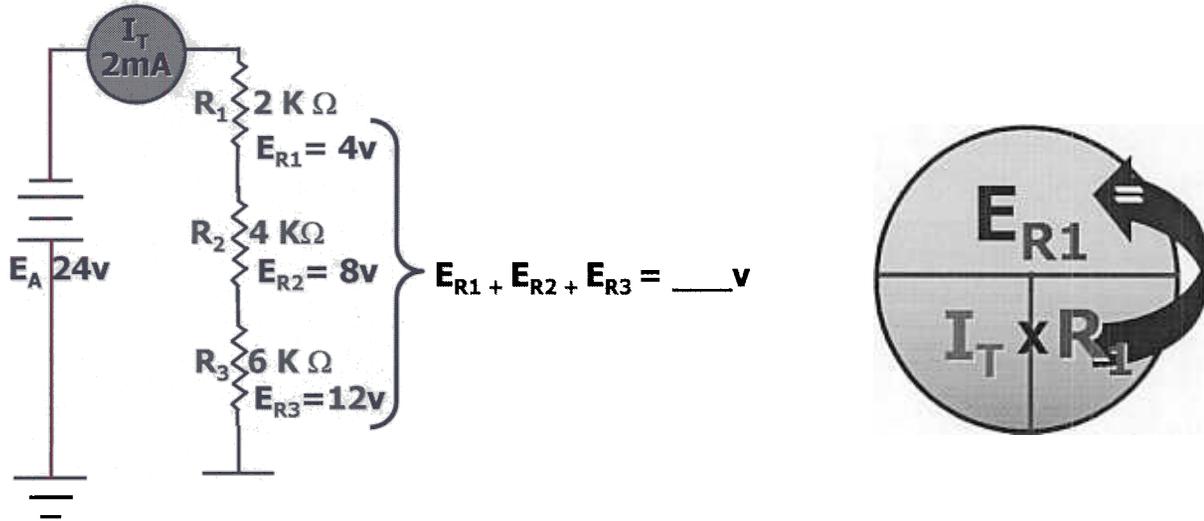**Kirchhoff's Law for Voltage; The sum of the individual voltage drops =**



The Largest Resistor drops the \_\_\_\_\_ voltage & the Smallest Resistor the \_\_\_\_\_

Solve for the voltage value.

$$3\text{mA} * 12\text{K}\Omega = \underline{\hspace{2cm}} \quad 5\text{mA} * 26\text{K}\Omega = \underline{\hspace{2cm}} \quad 2\text{A} * 36\Omega = \underline{\hspace{2cm}}$$

What is the relationship between Resistance and Current?

What is the relationship between Voltage and Current?


Solve for the current value.

$$24\text{V} / 6\text{K}\Omega = \underline{\hspace{2cm}} \quad 40\text{V} / 5\text{K}\Omega = \underline{\hspace{2cm}} \quad 18\text{V} / 3\text{K}\Omega = \underline{\hspace{2cm}}$$

What are the types of resistors? \_\_\_\_\_ & \_\_\_\_\_


Solve for the resistance value given the following information.
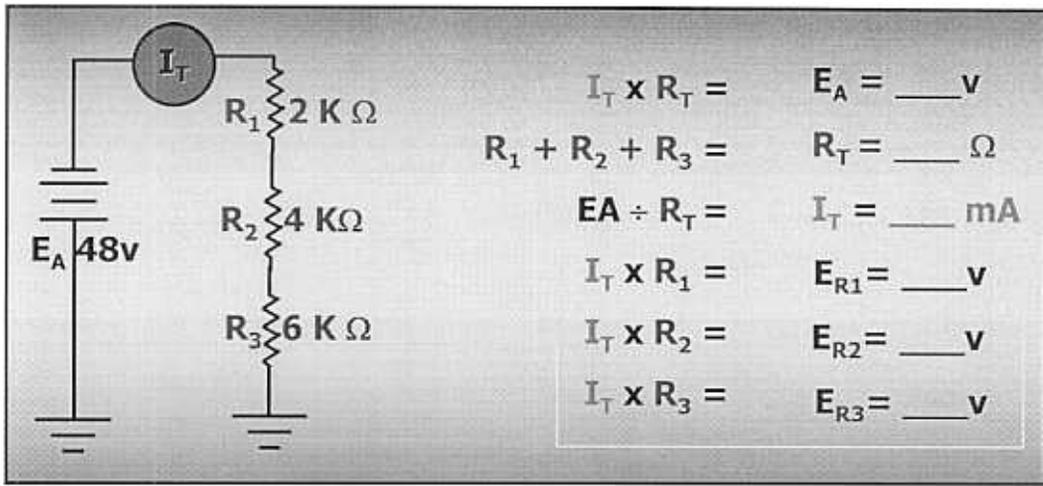
$$11\text{V} / 2.5\text{mA} = \underline{\hspace{2cm}} \quad 100\text{V} / 5\text{A} = \underline{\hspace{2cm}} \quad 80\text{V} / 3.5\text{mA} = \underline{\hspace{2cm}}$$



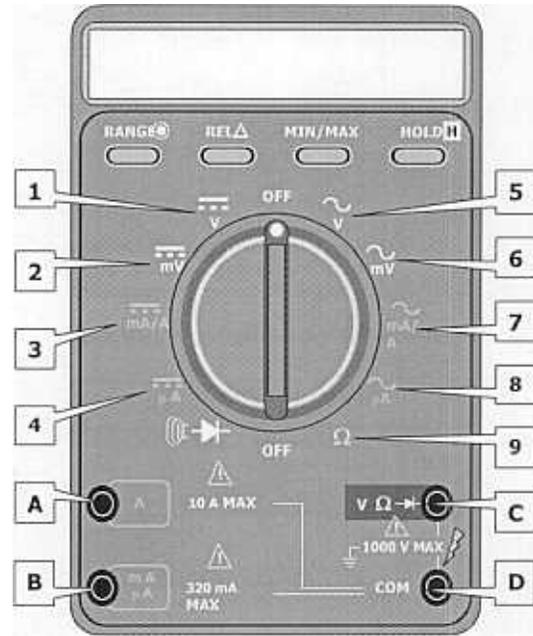**DC: Care & Use Multimeter**

Set the meter up to make the following types of measurement:



- 100VDC Selector switch to \_\_\_\_\_
- 100KΩ Selector switch to \_\_\_\_\_
- 10mA AC Selector switch to \_\_\_\_\_
- 60VAC Selector switch to \_\_\_\_\_
- 35 μA AC Selector switch to \_\_\_\_\_
- 20VAC Selector switch to \_\_\_\_\_
- 10KΩ Selector switch to \_\_\_\_\_
- 30mVAC Selector switch to \_\_\_\_\_
- 3A AC Selector switch to \_\_\_\_\_
- 26 μA DC Selector switch to \_\_\_\_\_
- 50mVDC Selector switch to \_\_\_\_\_

- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_
- Red probe \_\_\_\_\_

- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_
- Black Probe \_\_\_\_\_

Travel Position Selector switch to \_\_\_\_\_

**DC: Series Circuits**

A Series Circuit is defined as Ckt that has only \_\_\_\_\_ for current flow.


Draw arrows to indicate the correct relationships.

<b>E</b>	<b>I</b>	Direct	<b>R</b> Remains Constant
<b>R</b>	<b>I</b>	Inverse	<b>E</b> Remains Constant
<b>R</b>	<b>E<sub>R</sub></b>	Direct	

Resistors in Series are


$R_T$  is the \_\_\_\_\_ of the individual resistors in a series Ckt.

Solve for the following:

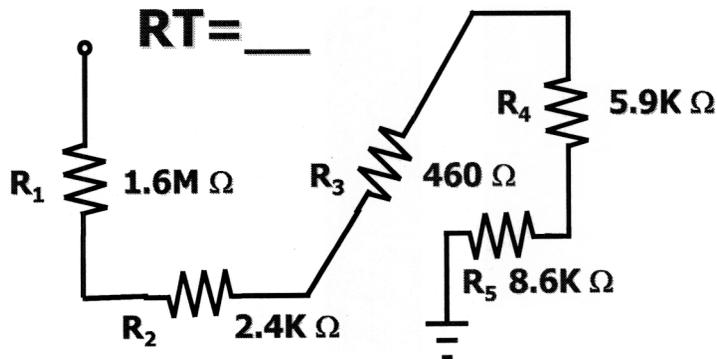

Voltage drops in Series are \_\_\_\_\_ to solve for Applied Voltage.

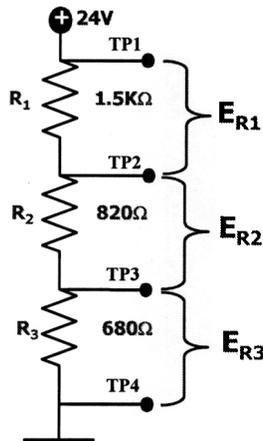EA is the \_\_\_\_\_ of the individual voltage drops in a series Ckt.



$$E_A$$

$$R_T \text{ --- } R_1 + R_2 + R_3$$

$$I_T \text{ --- } E_A \div R_T$$

$$E_{R1} \text{ --- } I_T \times R_1$$

$$E_{R2} \text{ --- } I_T \times R_2$$

$$E_{R3} \text{ --- } I_T \times R_3$$


IF two or more Resistors are of the same value then they will have the \_\_\_\_\_ voltage Drop.

If all the resistors are of the same Value, & EA is known then  $E_A \div \text{Number of Resistors} = E_{R\#}$ . True or False?

Voltages at Test Points are made in reference to \_\_\_\_\_

The voltages at TP are the \_\_\_\_\_ of the voltage Drops Between the TP & Gnd.

Solve for the following:

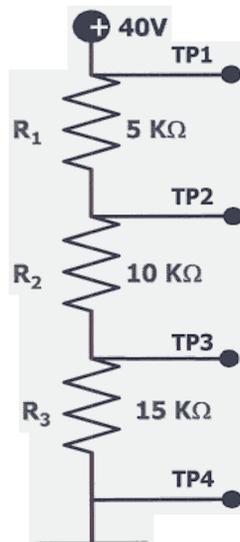

**F**

$$E_{R1} =$$

$$E_{R2} =$$

$$E_{R3} =$$

$$E_{TP1} = \text{---}$$

$$E_{TP2} = \text{---}$$

$$E_{TP3} = \text{---}$$

$$E_{TP4} =$$

Current flow in a series Ckt remains

Current is calculated by EA over

Current flows from the most potential to the most

If there is  $K\Omega$  of Resistance, there will be of Current.

Solve for the following:

$$12V / 6 K\Omega =$$

$$24V / 3 K\Omega =$$

$$60V / 25 K\Omega =$$

---

### DC: Series Circuits Trouble Shooting

4 basic principles in the approach to troubleshooting:

\_\_\_\_\_

Symptom: A measurement or an obvious indication, which when compared to the normal, is \_\_\_\_\_ or \_\_\_\_\_ to its normal operating parameters


The path has been severed in that component or Ckt. (Open , Short, Changed Value).

The device acts like a piece of wire. (Open , Short, Changed Value).


A component operates outside of it's specified value & tolerance (Open , Short, Changed Value).

Malfunction: Is simply defined based on the symptoms as an \_\_\_\_\_, or \_\_\_\_\_ value.

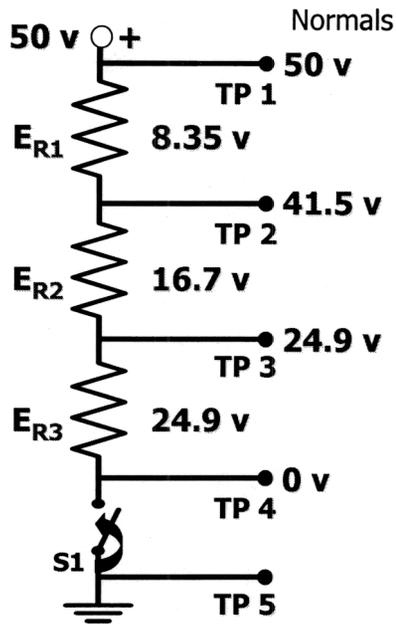Solve for the following malfunction symptoms




A. Symptoms

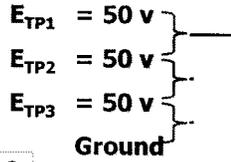


Malfunction:  
\_\_\_\_\_

C. Symptoms

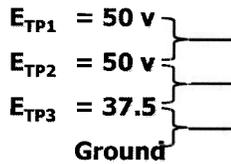

Malfunction:  
\_\_\_\_\_

B. Symptoms


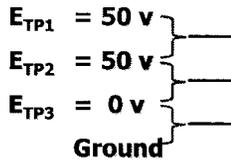



Malfunction:  
\_\_\_\_\_

DC: Parallel Circuits

A PARALLEL CKT is defined as an electrical circuit having \_\_\_\_\_

The 3 formulas for solving for REQ are

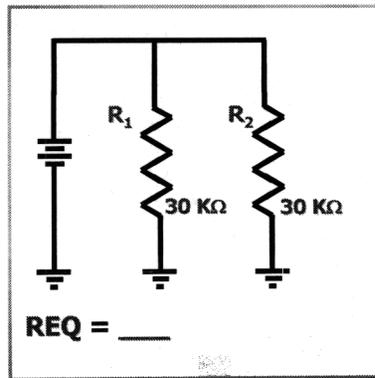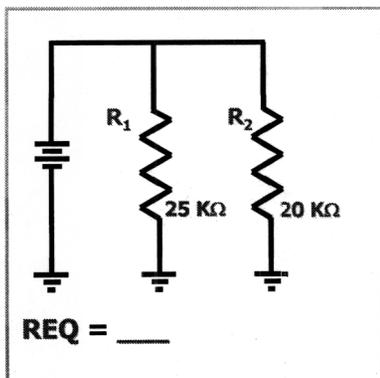

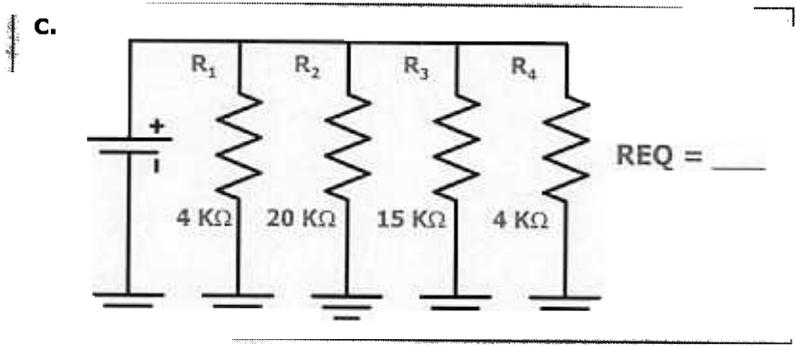


Voltage is \_\_\_\_\_ in a parallel Ckt.

In a parallel CKT,  $E_{REQ} / \text{ } = I_{R1}$

In a parallel CKT,  $REQ * I_T =$

The Sum of the Branch Currents is =


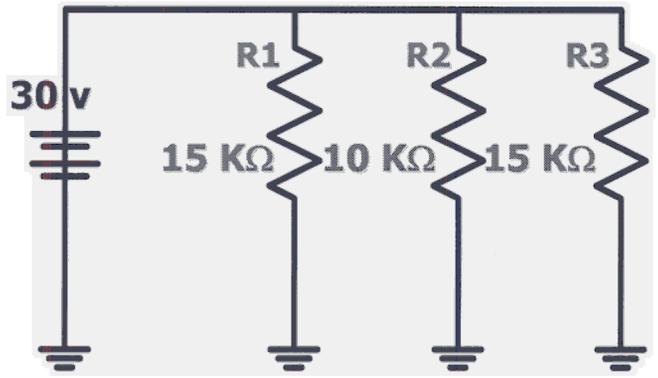
$E_A$  &  $E_{REQ}$  are the \_\_\_\_\_ in a Pure Parallel Ckt.



- $E_A =$
- $REQ =$
- $I_T = E_A \div REQ$
- $E_{R1} =$
- $E_{R2} = I_T \times REQ$
- $E_{R3} =$
- $I_{R1} = E_{REQ} \div R_1$
- $I_{R2} = E_{REQ} \div R_2$
- $I_{R3} = E_{REQ} \div R_3$

The Smallest Resistor Carries the \_\_\_\_\_ Current.

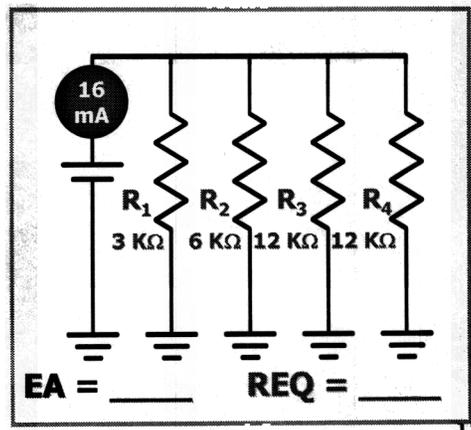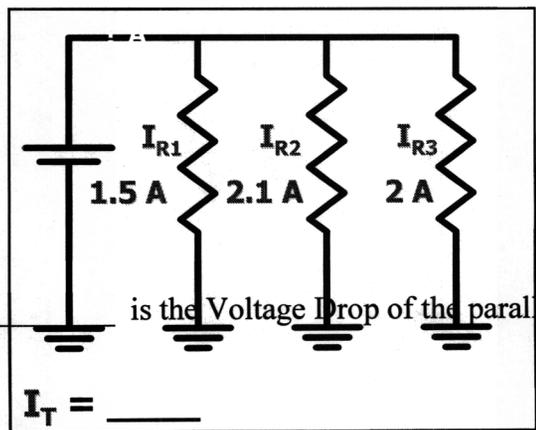The largest Resistor Carries the \_\_\_\_\_



**DC: Parallel Circuits Trouble Shooting**

EA & EREQ are the \_\_\_\_\_ in a PURE Parallel Ckt.

The REQ will always be \_\_\_\_\_ than the smallest resistor in the Ckt.


3 Methods of calculating REQ;

- ① \_\_\_\_\_, ② \_\_\_\_\_, ③ \_\_\_\_\_

Solve for the following reading across the open switch:

Solve for the following Malfunction:

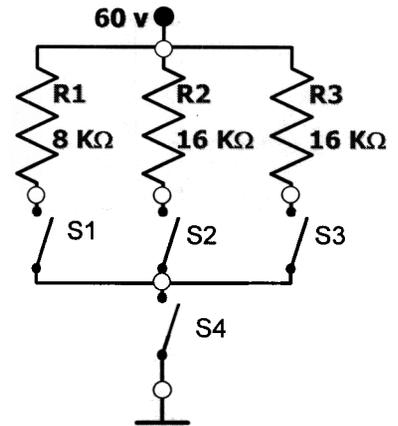- Reading across S1 current = 0mA
- Reading across S4 current = 11.25mA
- Reading across S2 current = 3.75mA
- Reading across S4 current = 7.5mA
- Reading across S2 current = 3.75mA




Current always takes the path of \_\_\_\_\_ Resistance.

Branch Current is \_\_\_\_\_ in a parallel CKT and =  $I_T$

Solve for the following:  
Malfunction

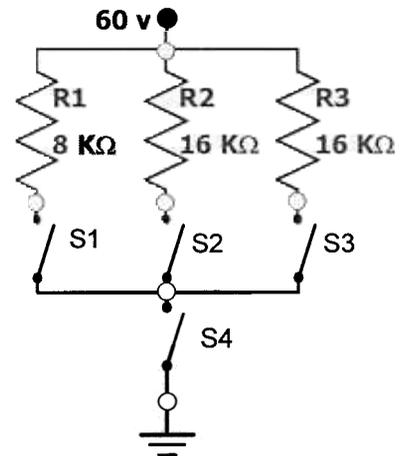- All switches are closed and REQ = 8KΩ
- S3 & S4 switches closed REQ =  $\infty\Omega$
- All switches are closed and REQ decreased
- S2, S3 & S4 switches closed REQ = 8KΩ
- All switches are closed and REQ increased
- S2, S3 & S4 switches closed REQ = 8KΩ
- All switches are closed and REQ decreased
- S2 & S4 switches closed REQ = 0KΩ




**DC: Series - Parallel Ckts**

**Series Rules:**




Resistance is \_\_\_\_\_ to =  $R_T$   
 Voltage is the \_\_\_\_\_ of the Resistors Voltage Drops [ER#], to = EA.  
 Current is \_\_\_\_\_, the same throughout the Ckt to =  $I_T$ .

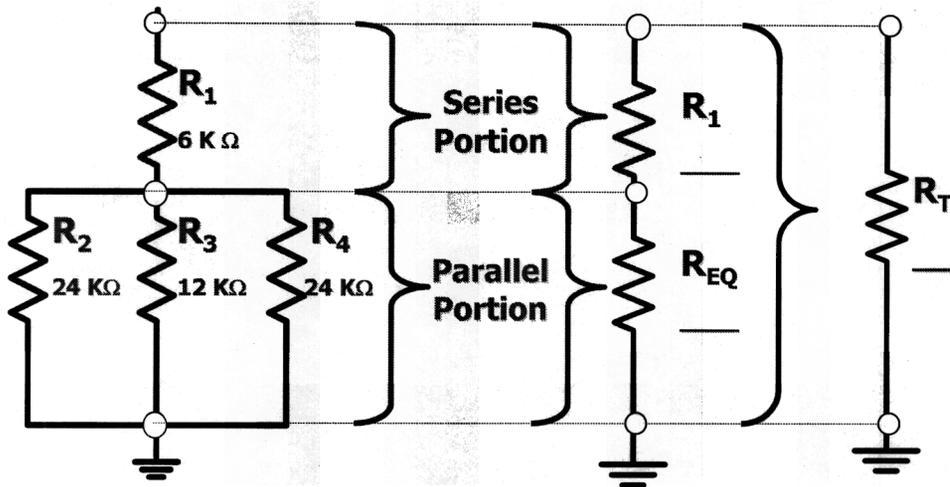**Parallel:**


Resistance is an Equivalency, called the \_\_\_\_\_  
 Voltage is \_\_\_\_\_ on each of the Branches, and is called the  
 Current is \_\_\_\_\_, the sum of the Branch currents is = to  $I_T$ .



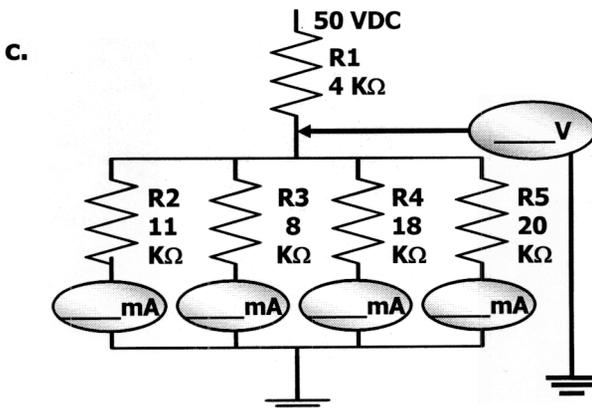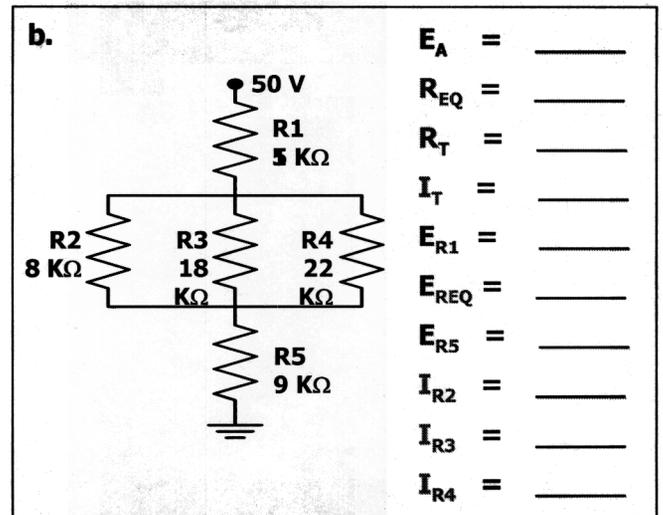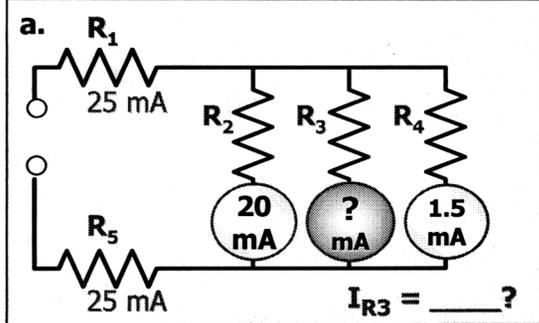Calculate for the Branch Current of  $R_3$ , [ $I_{R3}$ ].



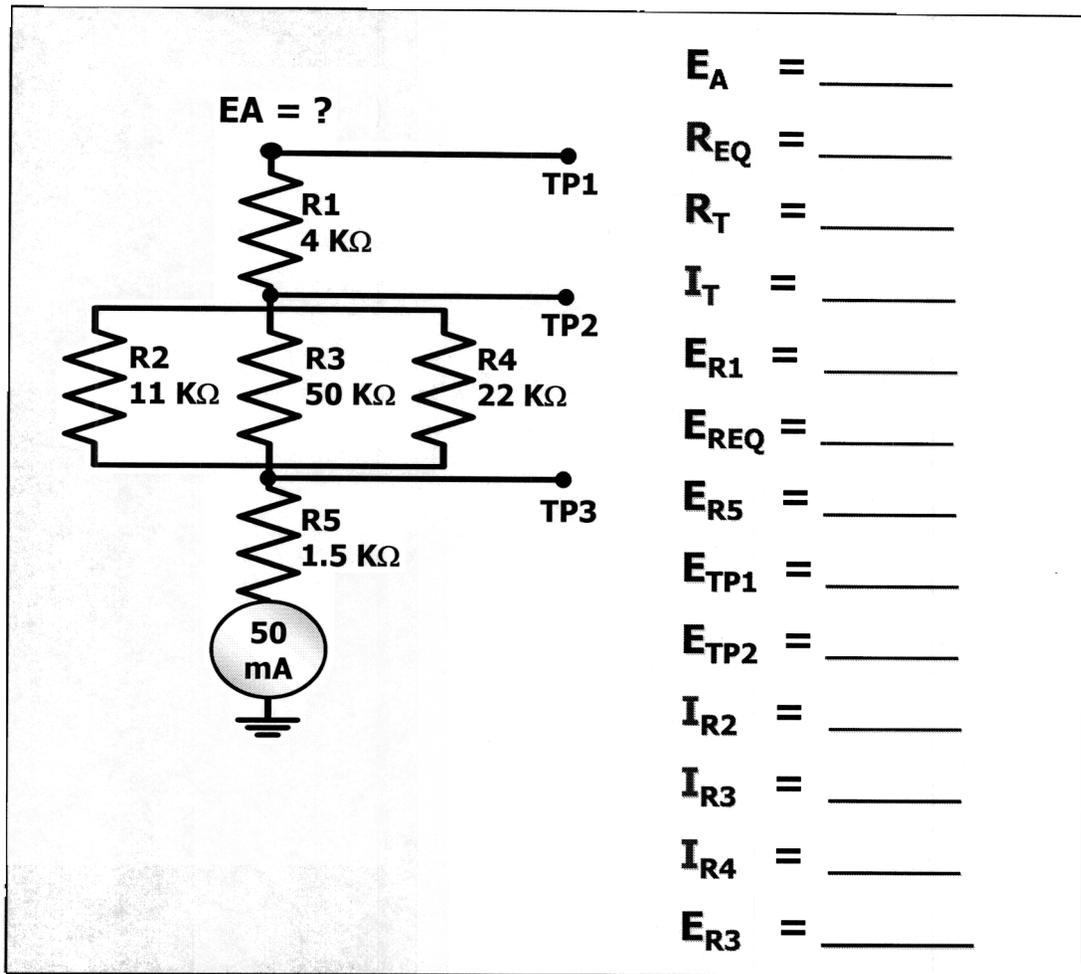$R_{EQ} =$   
 $R_T =$   
 $I_T =$   
 $E_{R1} =$



Malfunction

Symptom

$R_T = \infty \Omega$      $R_{EQ} = 6.3 K\Omega$      $I_T = 0mA$      $R1 = 4k\Omega$

$R_T = 23K\Omega$      $R_{EQ} = 0 K\Omega$      $I_{R2} = 0mA$      $I_{R3} = 0mA$

$R_T = \infty \Omega$      $R_{EQ} = 6.3K\Omega$      $I_{R3} = 0mA$      $R1 = \infty K\Omega$

$R_T = 7.8K\Omega$      $R_{EQ} = 6.3 K\Omega$      $I_T = 75.6mA$      $R1 = 15k\Omega$